

DDS ACADEMY

ALTERNATING CURRENT

DPP-1

(JEE MAINS)

EXERCISE 1

1. The power is transmitted from a power house on high voltage ac because
 - (a) Electric current travels faster at higher *volts*
 - (b) It is more economical due to less power wastage
 - (c) It is difficult to generate power at low voltage
 - (d) Chances of stealing transmission lines are minimized
2. The potential difference V and the current i flowing through an instrument in an ac circuit of frequency f are given by $V = 5 \cos \omega t$ volts and $I = 2 \sin \omega t$ amperes (where $\omega = 2\pi f$). The power dissipated in the instrument is
 - (a) Zero
 - (b) 10 W
 - (c) 5 W
 - (d) 2.5 W
3. In an ac circuit, V and I are given by
$$V = 100 \sin (100 t) \text{ volts}, I = 100 \sin \left(100 t + \frac{\pi}{3} \right) \text{ mA}$$
. The power dissipated in circuit is
 - (a) 10^4 watt
 - (b) 10 watt
 - (c) 2.5 watt
 - (d) 5 watt
4. Alternating current can not be measured by dc ammeter because
 - (a) ac cannot pass through dc ammeter
 - (b) Average value of complete cycle is zero
 - (c) ac is virtual
 - (d) ac changes its direction
5. The resistance of a coil for dc is in ohms. In ac, the resistance
 - (a) Will remain same
 - (b) Will increase
 - (c) Will decrease
 - (d) Will be zero
6. If instantaneous current is given by $i = 4 \cos (\omega t + \phi)$ amperes, then the *r.m.s.* value of current is
 - (a) 4 amperes
 - (b) $2\sqrt{2}$ amperes
 - (c) $4\sqrt{2}$ amperes
 - (d) Zero amperes
7. In an ac circuit, peak value of voltage is 423 volts. Its effective voltage is
 - (a) 400 volts
 - (b) 323 volts
 - (c) 300 volts
 - (d) 340 volts
8. In an ac circuit $I = 100 \sin 200 \pi t$. The time required for the current to achieve its peak value will be
 - (a) $\frac{1}{100}$ sec
 - (b) $\frac{1}{200}$ sec
 - (c) $\frac{1}{300}$ sec
 - (d) $\frac{1}{400}$ sec
9. The peak value of an Alternating current is 6 amp, then *r.m.s.* value of current will be
 - (a) 3 A
 - (b) $3\sqrt{3}$ A
 - (c) $3\sqrt{2}$ A
 - (d) $2\sqrt{3}$ A
10. A generator produces a voltage that is given by $V = 240 \sin 120 t$, where t is in seconds. The frequency and *r.m.s.* voltage are
 - (a) 60 Hz and 240 V
 - (b) 19 Hz and 120 V
 - (c) 19 Hz and 170 V
 - (d) 754 Hz and 70 V
11. If E_0 represents the peak value of the voltage in an ac circuit, the *r.m.s.* value of the voltage will be
 - (a) $\frac{E_0}{\pi}$
 - (b) $\frac{E_0}{2}$

(c) $\frac{E_0}{\sqrt{\pi}}$ (d) $\frac{E_0}{\sqrt{2}}$

12. The peak value of 220 volts of ac mains is

- (a) 155.6 volts (b) 220.0 volts
(c) 311.0 volts (d) 440 volts

13. A sinusoidal ac current flows through a resistor of resistance R . If the peak current is I_p , then the power dissipated is

- (a) $I_p^2 R \cos \theta$ (b) $\frac{1}{2} I_p^2 R$
(c) $\frac{4}{\pi} I_p^2 R$ (d) $\frac{1}{\pi} I_p^2 R$

14. A 40Ω electric heater is connected to a 200 V, 50 Hz mains supply. The peak value of electric current flowing in the circuit is approximately

- (a) 2.5 A (b) 5.0 A
(c) 7 A (d) 10 A

15. The frequency of ac mains in India is

- (a) 30 c/s or Hz (b) 50 c/s or Hz
(c) 60 c/s or Hz (d) 120 c/s or Hz

16. The r.m.s. value of an ac of 50 Hz is 10 amp. The time taken by the alternating current in reaching from zero to maximum value and the peak value of current will be

- (a) 2×10^{-2} sec and 14.14 amp
(b) 1×10^{-2} sec and 7.07 amp
(c) 5×10^{-3} sec and 7.07 amp
(d) 5×10^{-3} sec and 14.14 amp

17. The root mean square value of the alternating current is equal to

- (a) Twice the peak value
(b) Half the peak value
(c) $\frac{1}{\sqrt{2}}$ times the peak value
(d) Equal to the peak value

18. The peak value of an alternating e.m.f. E is given by $E = E_0 \cos \omega t$ is 10 volts and its frequency is 50 Hz. At time

$t = \frac{1}{600}$ sec, the instantaneous e.m.f. is

- (a) 10 V (b) $5\sqrt{3}$ V
(c) 5 V (d) 1 V

19. If a current I given by $I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$ flows in an ac circuit across which an ac potential of $E = E_0 \sin \omega t$ has been applied, then the power consumption P in the circuit will be

- (a) $P = \frac{E_0 I_0}{\sqrt{2}}$ (b) $P = \sqrt{2} E_0 I_0$
(c) $P = \frac{E_0 I_0}{2}$ (d) $P = 0$

20. In an ac circuit, the instantaneous values of e.m.f. and current are $e = 200 \sin 314 t$ volt and $i = \sin\left(314 t + \frac{\pi}{3}\right)$ ampere. The average power consumed in watt is

- (a) 200 (b) 100
(c) 50 (d) 25

21. An ac generator produced an output voltage $E = 170 \sin 377 t$ volts, where t is in seconds. The frequency of ac voltage is
- (a) 50 Hz (b) 110 Hz
(c) 60 Hz (d) 230 Hz
22. In general in an alternating current circuit
- (a) The average value of current is zero
(b) The average value of square of the current is zero
(c) Average power dissipation is zero
(d) The phase difference between voltage and current is zero
23. An alternating current is given by the equation $i = i_1 \cos \omega t + i_2 \sin \omega t$. The r.m.s. current is given by
- (a) $\frac{1}{\sqrt{2}}(i_1 + i_2)$ (b) $\frac{1}{\sqrt{2}}(i_1 + i_2)^2$
(c) $\frac{1}{\sqrt{2}}(i_1^2 + i_2^2)^{1/2}$ (d) $\frac{1}{2}(i_1^2 + i_2^2)^{1/2}$
24. In an ac circuit, the current is given by $i = 5 \sin \left(100 t - \frac{\pi}{2} \right)$ and the ac potential is $V = 200 \sin(100)t$ volt. Then the power consumption is
- (a) 20 watts (b) 40 watts
(c) 1000 watts (d) 0 watt
25. An electric lamp is connected to 220 V, 50 Hz supply. Then the peak value of voltage is
- (a) 210 V (b) 211 V
(c) 311 V (d) 320 V
26. In a circuit, the value of the alternating current is measured by hot wire ammeter as 10 ampere. Its peak value will be
- (a) 10 A (b) 20 A
(c) 14.14 A (d) 7.07 A
27. The voltage of domestic ac is 220 volt. What does this represent
- (a) Mean voltage
(b) Peak voltage
(c) Root mean voltage
(d) Root mean square voltage
28. The r.m.s. voltage of domestic electricity supply is 220 volt. Electrical appliances should be designed to withstand an instantaneous voltage of
- (a) 220 V (b) 310 V
(c) 330 V (d) 440 V
29. The process by which ac is converted into dc is known as
- (a) Purification (b) Amplification
(c) Rectification (d) Current amplification
30. In an ac circuit with voltage V and current I , the power dissipated is
- (a) VI
(b) $\frac{1}{2} VI$
(c) $\frac{1}{\sqrt{2}} VI$
(d) Depends on the phase between V and I
31. For an ac circuit $V = 15 \sin \omega t$ and $I = 20 \cos \omega t$ the average power consumed in this circuit is
- (a) 300 Watt (b) 150 Watt
(c) 75 Watt (d) zero
32. A bulb is connected first with dc and then ac of same voltage then it will shine brightly with
- (a) AC
(b) DC

- (c) Brightness will be in ratio 1/1.4
(d) Equally with both
33. An ac supply gives 30 V *r.m.s.* which passes through a $10\ \Omega$ resistance. The power dissipated in it is
(a) $90\sqrt{2}\ W$ (b) $90\ W$
(c) $45\sqrt{2}\ W$ (d) $45\ W$
34. The frequency of an alternating voltage is 50 *cycles/sec* and its amplitude is 120V. Then the *r.m.s.* value of voltage is
(a) 101.3V (b) 84.8V
(c) 70.7V (d) 56.5V
35. A resistance of 20 *ohms* is connected to a source of an alternating potential $V = 220 \sin(100\pi t)$. The time taken by the current to change from its peak value to *r.m.s* value is
(a) 0.2 *sec* (b) 0.25 *sec*
(c) $25 \times 10^{-3}\ sec$ (d) $2.5 \times 10^{-3}\ sec$
36. Voltage and current in an ac circuit are given by $V = 5 \sin\left(100\pi t - \frac{\pi}{6}\right)$ and $I = 4 \sin\left(100\pi t + \frac{\pi}{6}\right)$
(a) Voltage leads the current by 30°
(b) Current leads the voltage by 30°
(c) Current leads the voltage by 60°
(d) Voltage leads the current by 60°
37. If an ac main supply is given to be 220 V. What would be the average e.m.f. during a positive half cycle
(a) 198V (b) 386V
(c) 256V (d) None of these
38. In an ac circuit, the *r.m.s.* value of current, I_{rms} is related to the peak current, I_0 by the relation
(a) $I_{rms} = \frac{1}{\pi} I_0$ (b) $I_{rms} = \frac{1}{\sqrt{2}} I_0$
(c) $I_{rms} = \sqrt{2} I_0$ (d) $I_{rms} = \pi I_0$
39. An alternating voltage is represented as $E = 20 \sin 300t$. The average value of voltage over one cycle will be
(a) Zero (b) 10 *volt*
(c) $20\sqrt{2}\ volt$ (d) $\frac{20}{\sqrt{2}}\ volt$
40. The ratio of peak value and *r.m.s* value of an alternating current is
(a) 1 (b) $\frac{1}{2}$
(c) $\sqrt{2}$ (d) $1/\sqrt{2}$
41. A 280 *ohm* electric bulb is connected to 200V electric line. The peak value of current in the bulb will be
(a) About one ampere (b) Zero
(c) About two ampere (d) About four ampere
42. An ac source is rated at 220V, 50 *Hz*. The time taken for voltage to change from its peak value to zero is
(a) 50 *sec* (b) 0.02 *sec*
(c) 5 *sec* (d) $5 \times 10^{-3}\ sec$
43. If the value of potential in an ac, circuit is 10V, then the peak value of potential is
(a) $\frac{10}{\sqrt{2}}$ (b) $10\sqrt{2}$
(c) $20\sqrt{2}$ (d) $\frac{20}{\sqrt{2}}$

44. A lamp consumes only 50% of peak power in an a.c. circuit. What is the phase difference between the applied voltage and the circuit current
- (a) $\frac{\pi}{6}$ (b) $\frac{\pi}{3}$
 (c) $\frac{\pi}{4}$ (d) $\frac{\pi}{2}$
45. If an alternating voltage is represented as $E = 141 \sin(628 t)$, then the *rms* value of the voltage and the frequency are respectively
- (a) 141 V, 628 Hz (b) 100 V, 50 Hz
 (c) 100 V, 100 Hz (d) 141 V, 100 Hz
46. The maximum value of a.c. voltage in a circuit is 707V. Its *rms* value is
- (a) 70.7 V (b) 100 V
 (c) 500 V (d) 707 V

EXERCISE 2

- Choke coil works on the principle of
 - Transient current
 - Self induction
 - Mutual induction
 - Wattless current
- A choke coil has
 - High inductance and low resistance
 - Low inductance and high resistance
 - High inductance and high resistance
 - Low inductance and low resistance
- Choke coil is used to control
 - ac
 - dc
 - Both ac and dc
 - Neither ac nor dc
- Current in the circuit is wattless, if
 - Inductance in the circuit is zero
 - Resistance in the circuit is zero
 - Current is alternating
 - Resistance and inductance both are zero
- The phase angle between e.m.f. and current in *LCR* series ac circuit is
 - 0 to $\pi/2$
 - $\pi/4$
 - $\pi/2$
 - π
- A choke coil is preferred to a rheostat in ac circuit as
 - It consumes almost zero power
 - It increases current
 - It increases power
 - It increases voltage
- An alternating e.m.f. is applied to purely capacitive circuit. The phase relation between e.m.f. and current flowing in the circuit is **or**
 In a circuit containing capacitance only
 - e.m.f. is ahead of current by $\pi/2$
 - Current is ahead of e.m.f. by $\pi/2$
 - Current lags behind e.m.f. by π
 - Current is ahead of e.m.f. by π
- An ac source is connected to a resistive circuits. Which of the following is true
 - Current leads the voltage and both are in same phase
 - Current lags behind the voltage and both are in same phase
 - Current and voltage are in same phase
 - Any of the above may be true depending upon the value of resistance
- The average power dissipated in a pure inductor of inductance L when an ac current is passing through it, is

- (a) $\frac{1}{2} LI^2$ (b) $\frac{1}{4} LI^2$
 (c) $2 LI^2$ (d) Zero
 (Inductance of the coil L and current I)
10. An alternating current of frequency ' f ' is flowing in a circuit containing a resistance R and a choke L in series. The impedance of this circuit is
 (a) $R + 2\pi fL$ (b) $\sqrt{R^2 + 4\pi^2 f^2 L^2}$
 (c) $\sqrt{R^2 + L^2}$ (d) $\sqrt{R^2 + 2\pi fL}$
11. A resonant ac circuit contains a capacitor of capacitance $10^{-6} F$ and an inductor of $10^{-4} H$. The frequency of electrical oscillations will be
 (a) $10^5 Hz$ (b) $10 Hz$
 (c) $\frac{10^5}{2\pi} Hz$ (d) $\frac{10}{2\pi} Hz$
12. Power delivered by the source of the circuit becomes maximum, when
 (a) $\omega L = \omega C$ (b) $\omega L = \frac{1}{\omega C}$
 (c) $\omega L = -\left(\frac{1}{\omega C}\right)^2$ (d) $\omega L = \sqrt{\omega C}$
13. An alternating voltage is connected in series with a resistance R and an inductance L . If the potential drop across the resistance is $200 V$ and across the inductance is $150 V$, then the applied voltage is
 (a) $350 V$ (b) $250 V$
 (c) $500 V$ (d) $300 V$
14. An inductive circuit contains resistance of 10Ω and an inductance of $20 H$. If an ac voltage of $120 V$ and frequency $60 Hz$ is applied to this circuit, the current would be nearly
 (a) $0.32 amp$ (b) $0.016 amp$
 (c) $0.48 amp$ (d) $0.80 amp$
15. Same current is flowing in two alternating circuits. The first circuit contains only inductance and the other contains only a capacitor. If the frequency of the e.m.f. of ac is increased, the effect on the value of the current will be
 (a) Increases in the first circuit and decreases in the other
 (b) Increases in both the circuits
 (c) Decreases in both the circuits
 (d) Decreases in the first circuit and increases in the other
16. A capacitor is a perfect insulator for
 (a) Alternating currents (b) Direct currents
 (c) Both ac and dc (d) None of these
17. In a circuit containing an inductance of zero resistance, the e.m.f. of the applied ac voltage leads the current by
 (a) 90° (b) 45°
 (c) 30° (d) 0°
18. In a pure inductive circuit or In an ac circuit containing inductance only, the current
 (a) Leads the e.m.f. by 90°
 (b) Lags behind the e.m.f. by 90°
 (c) Sometimes leads and sometime lags behind the e.m.f.
 (d) Is in phase with the e.m.f.
19. A $20 volts$ ac is applied to a circuit consisting of a resistance and a coil with negligible resistance. If the voltage across the resistance is $12 V$, the voltage across the coil is
 (a) $16 volts$ (b) $10 volts$
 (c) $8 volts$ (d) $6 volts$

20. A resistance of $300\ \Omega$ and an inductance of $\frac{1}{\pi}$ henry are connected in series to a ac voltage of 20 volts and 200 Hz frequency. The phase angle between the voltage and current is
- (a) $\tan^{-1} \frac{4}{3}$ (b) $\tan^{-1} \frac{3}{4}$
 (c) $\tan^{-1} \frac{3}{2}$ (d) $\tan^{-1} \frac{2}{5}$
21. The power factor of LCR circuit at resonance is
- (a) 0.707 (b) 1
 (c) Zero (d) 0.5
22. An inductance of 1 mH a condenser of $10\ \mu F$ and a resistance of $50\ \Omega$ are connected in series. The reactances of inductor and condensers are same. The reactance of either of them will be
- (a) $100\ \Omega$ (b) $30\ \Omega$
 (c) $3.2\ \Omega$ (d) $10\ \Omega$
23. The natural frequency of a L-C circuit is equal to
- (a) $\frac{1}{2\pi} \sqrt{LC}$ (b) $\frac{1}{2\pi\sqrt{LC}}$
 (c) $\frac{1}{2\pi} \sqrt{\frac{L}{C}}$ (d) $\frac{1}{2\pi} \sqrt{\frac{C}{L}}$
24. An alternating voltage $E = 200\sqrt{2} \sin(100\ t)$ is connected to a 1 microfarad capacitor through an ac ammeter. The reading of the ammeter shall be
- (a) 10 mA (b) 20 mA
 (c) 40 mA (d) 80 mA
25. An ac circuit consists of an inductor of inductance 0.5 H and a capacitor of capacitance $8\ \mu F$ in series. The current in the circuit is maximum when the angular frequency of ac source is
- (a) 500 rad/sec (b) 2×10^5 rad/sec
 (c) 4000 rad/sec (d) 5000 rad/sec
26. The average power dissipation in a pure capacitance in ac circuit is
- (a) $\frac{1}{2} CV^2$ (b) CV^2
 (c) $\frac{1}{4} CV^2$ (d) Zero
27. In a region of uniform magnetic induction $B = 10^{-2}$ tesla , a circular coil of radius 30 cm and resistance π^2 ohm is rotated about an axis which is perpendicular to the direction of B and which forms a diameter of the coil. If the coil rotates at 200 rpm the amplitude of the alternating current induced in the coil is
- (a) $4\pi^2$ mA (b) 30 mA
 (c) 6 mA (d) 200 mA
28. An inductive circuit contains a resistance of 10 ohm and an inductance of 2.0 henry. If an ac voltage of 120 volt and frequency of 60 Hz is applied to this circuit, the current in the circuit would be nearly
- (a) 0.32 amp (b) 0.16 amp
 (c) 0.48 amp (d) 0.80 amp
29. In a LCR circuit having $L = 8.0$ henry, $C = 0.5\ \mu F$ and $R = 100$ ohm in series. The resonance frequency in per second is
- (a) 600 radian (b) 600 Hz
 (c) 500 radian (d) 500 Hz
30. In LCR circuit, the capacitance is changed from C to 4C. For the same resonant frequency, the inductance should be changed from L to
- (a) 2L (b) $L/2$
 (c) $L/4$ (d) 4L
31. A 120 volt ac source is connected across a pure inductor of inductance 0.70 henry. If the frequency of the source is 60 Hz, the current passing through the inductor is

- (a) 4.55 *amps* (b) 0.355 *amps*
(c) 0.455 *amps* (d) 3.55 *amps*
32. The impedance of a circuit consists of 3 *ohm* resistance and 4 *ohm* reactance. The power factor of the circuit is
(a) 0.4 (b) 0.6
(c) 0.8 (d) 1.0
33. L , C and R denote inductance, capacitance and resistance respectively. Pick out the combination which does not have the dimensions of frequency
(a) $\frac{1}{RC}$ (b) $\frac{R}{L}$
(c) $\frac{1}{\sqrt{LC}}$ (d) $\frac{C}{L}$
34. The power factor of a good choke coil is
(a) Nearly zero (b) Exactly zero
(c) Nearly one (d) Exactly one
35. If resistance of 100 Ω , inductance of 0.5 *henry* and capacitance of $10 \times 10^{-6} F$ are connected in series through 50 *Hz* ac supply, then impedance is
(a) 1.876 (b) 18.76
(c) 189.72 (d) 101.3
36. An alternating current source of frequency 100 *Hz* is joined to a combination of a resistance, a capacitance and a coil in series. The potential difference across the coil, the resistance and the capacitor is 46, 8 and 40 *volt* respectively. The electromotive force of alternating current source in *volt* is
(a) 94 (b) 14
(c) 10 (d) 76
37. A 10 *ohm* resistance, 5 *mH* coil and 10 μF capacitor are joined in series. When a suitable frequency alternating current source is joined to this combination, the circuit resonates. If the resistance is halved, the resonance frequency
(a) Is halved (b) Is doubled
(c) Remains unchanged (d) Is quadrupled
38. L , C and R represent physical quantities inductance, capacitance and resistance respectively. The combination representing dimension of frequency is
(a) LC (b) $(LC)^{-1/2}$
(c) $\left(\frac{L}{C}\right)^{-1/2}$ (d) $\frac{C}{L}$
39. In a series circuit $R = 300 \Omega$, $L = 0.9 H$, $C = 2.0 \mu F$ and $\omega = 1000 \text{ rad/sec}$. The impedance of the circuit is
(a) 1300 Ω (b) 900 Ω
(c) 500 Ω (d) 400 Ω
40. In a L - R circuit, the value of L is $\left(\frac{0.4}{\pi}\right)$ *henry* and the value of R is 30 *ohm*. If in the circuit, an alternating *e.m.f.* of 200 *volt* at 50 cycles per sec is connected, the impedance of the circuit and current will be
(a) 11.4 Ω , 17.5 *A* (b) 30.7 Ω , 6.5 *A*
(c) 40.4 Ω , 5 *A* (d) 50 Ω , 4 *A*
41. The reactance of a coil when used in the domestic ac power supply (220 *volt*, 50 *cycles*) is 100 *ohm*. The self inductance of the coil is nearly
(a) 3.2 *henry* (b) 0.32 *henry*
(c) 2.2 *henry* (d) 0.22 *henry*
42. In a series LCR circuit, operated with an ac of angular frequency ω , the total impedance is
(a) $[R^2 + (L\omega - C\omega)^2]^{1/2}$

- (b) $\left[R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2 \right]^{1/2}$
- (c) $\left[R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2 \right]^{-1/2}$
- (d) $\left[(R\omega)^2 + \left(L\omega - \frac{1}{C\omega} \right)^2 \right]^{1/2}$

43. The reactance of a $25 \mu F$ capacitor at the ac frequency of 4000 Hz is

- (a) $\frac{5}{\pi} \text{ ohm}$ (b) $\sqrt{\frac{5}{\pi}} \text{ ohm}$
- (c) 10 ohm (d) $\sqrt{10} \text{ ohm}$

44. The frequency for which a $5 \mu F$ capacitor has a reactance of $\frac{1}{1000} \text{ ohm}$ is given by

- (a) $\frac{100}{\pi} \text{ MHz}$ (b) $\frac{1000}{\pi} \text{ Hz}$
- (c) $\frac{1}{1000} \text{ Hz}$ (d) 1000 Hz

45. An e.m.f. $E = 4 \cos(1000 t) \text{ volt}$ is applied to an LR-circuit of inductance 3 mH and resistance 4 ohms . The amplitude of current in the circuit is

- (a) $\frac{4}{\sqrt{7}} \text{ A}$ (b) 1.0 A
- (c) $\frac{4}{7} \text{ A}$ (d) 0.8 A

46. In an ac circuit, a resistance of $R \text{ ohm}$ is connected in series with an inductance L . If phase angle between voltage and current be 45° , the value of inductive reactance will be

- (a) $\frac{R}{4}$
- (b) $\frac{R}{2}$
- (c) R
- (d) Cannot be found with the given data

47. A coil of inductance L has an inductive reactance of X_L in an AC circuit in which the effective current is I . The coil is made from a super-conducting material and has no resistance. The rate at which power is dissipated in the coil is

- (a) 0 (b) IX_L
- (c) $I^2 X_L$ (d) IX_L^2

48. The phase difference between the current and voltage of LCR circuit in series combination at resonance is

- (a) 0 (b) $\pi / 2$
- (c) π (d) $-\pi$

49. In a series resonant circuit, the ac voltage across resistance R , inductance L and capacitance C are 5 V , 10 V and 10 V respectively. The ac voltage applied to the circuit will be

- (a) 20 V (b) 10 V
- (c) 5 V (d) 25 V

50. When 100 volt dc is applied across a coil, a current of 1 amp flows through it. When 100 volt ac at 50 cycle s^{-1} is applied to the same coil, only 0.5 ampere current flows. The impedance of the coil is

- (a) 100Ω (b) 200Ω
- (c) 300Ω (d) 400Ω

51. The coefficient of induction of a choke coil is $0.1H$ and resistance is $12\ \Omega$. If it is connected to an alternating current source of frequency $60\ Hz$, then power factor will be
 (a) 0.32 (b) 0.30
 (c) 0.28 (d) 0.24
52. For series LCR circuit, wrong statement is
 (a) Applied e.m.f. and potential difference across resistance are in same phase
 (b) Applied e.m.f. and potential difference at inductor coil have phase difference of $\pi/2$
 (c) Potential difference at capacitor and inductor have phase difference of $\pi/2$
 (d) Potential difference across resistance and capacitor have phase difference of $\pi/2$
53. In a purely resistive ac circuit, the current
 (a) Lags behind the e.m.f. in phase
 (b) Is in phase with the e.m.f.
 (c) Leads the e.m.f. in phase
 (d) Leads the e.m.f. in half the cycle and lags behind it in the other half
54. If an $8\ \Omega$ resistance and $6\ \Omega$ reactance are present in an ac series circuit then the impedance of the circuit will be
 (a) $20\ ohm$ (b) $5\ ohm$
 (c) $10\ ohm$ (d) $14\sqrt{2}\ ohm$
55. A $12\ ohm$ resistor and a 0.21 henry inductor are connected in series to an ac source operating at $20\ volts$, 50 cycle/second. The phase angle between the current and the source voltage is
 (a) 30° (b) 40°
 (c) 80° (d) 90°
56. What will be the phase difference between virtual voltage and virtual current, when the current in the circuit is wattless
 (a) 90° (b) 45°
 (c) 180° (d) 60°
57. The resonant frequency of a circuit is f . If the capacitance is made 4 times the initial values, then the resonant frequency will become
 (a) $f/2$ (b) $2f$
 (c) f (d) $f/4$
58. In the non-resonant circuit, what will be the nature of the circuit for frequencies higher than the resonant frequency
 (a) Resistive (b) Capacitive
 (c) Inductive (d) None of the above
59. In an ac circuit, the potential difference across an inductance and resistance joined in series are respectively $16\ V$ and $20\ V$. The total potential difference across the circuit is
 (a) $20.0\ V$ (b) $25.6\ V$
 (c) $31.9\ V$ (d) $53.5\ V$
60. A $220\ V$, $50\ Hz$ ac source is connected to an inductance of $0.2\ H$ and a resistance of $20\ ohm$ in series. What is the current in the circuit
 (a) $10\ A$ (b) $5\ A$
 (c) $33.3\ A$ (d) $3.33\ A$
61. An LCR circuit contains $R = 50\ \Omega$, $L = 1\ mH$ and $C = 0.1\ \mu F$. The impedance of the circuit will be minimum for a frequency of
 (a) $\frac{10^5}{2\pi}\ s^{-1}$ (b) $\frac{10^6}{2\pi}\ s^{-1}$
 (c) $2\pi \times 10^5\ s^{-1}$ (d) $2\pi \times 10^6\ s^{-1}$
62. In a series LCR circuit, resistance $R = 10\ \Omega$ and the impedance $Z = 20\ \Omega$. The phase difference between the current and the voltage is
 (a) 30° (b) 45°
 (c) 60° (d) 90°
63. A series ac circuit consist of an inductor and a capacitor. The inductance and capacitance is respectively $1\ henry$ and $25\ \mu F$. If the current is maximum in circuit then angular frequency will be
 (a) 200 (b) 100


- (c) 50 (d) $200/2\pi$

64. An alternating e.m.f. of frequency $\nu \left(= \frac{1}{2\pi\sqrt{LC}} \right)$ is applied to a series LCR circuit. For this frequency of the applied e.m.f.

- (a) The circuit is at resonance and its impedance is made up only of a reactive part
 (b) The current in the circuit is in phase with the applied e.m.f. and the voltage across R equals this applied emf
 (c) The sum of the p.d.'s across the inductance and capacitance equals the applied e.m.f. which is 180° ahead of phase of the current in the circuit
 (d) The quality factor of the circuit is $\omega L / R$ or $1 / \omega CR$ and this is a measure of the voltage magnification (produced by the circuit at resonance) as well as the sharpness of resonance of the circuit

65. In the circuit shown below, the ac source has voltage $V = 20 \cos(\omega t)$ volts with $\omega = 2000 \text{ rad/sec}$. the amplitude of the current will be nearest to

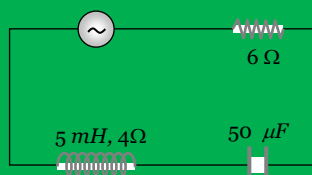- (a) 2A
 (b) 3.3A
 (c) $2/\sqrt{5} \text{ A}$
 (d) $\sqrt{5} \text{ A}$



66. The value of the current through an inductance of $1H$ and of negligible resistance, when connected through an ac source of 200 V and 50 Hz , is

- (a) 0.637A (b) 1.637A
 (c) 2.637A (d) 3.637A

67. The quality factor of LCR circuit having resistance (R) and inductance (L) at resonance frequency (ω) is given by

- (a) $\frac{\omega L}{R}$ (b) $\frac{R}{\omega L}$
 (c) $\left(\frac{\omega L}{R} \right)^{1/2}$ (d) $\left(\frac{\omega L}{R} \right)^2$

68. Power factor is maximum in an LCR circuit when

- (a) $X_L = X_C$ (b) $R = 0$
 (c) $X_L = 0$ (d) $X_C = 0$

69. In an ac circuit the reactance of a coil is $\sqrt{3}$ times its resistance, the phase difference between the voltage across the coil to the current through the coil will be

- (a) $\pi / 3$ (b) $\pi / 2$
 (c) $\pi / 4$ (d) $\pi / 6$

70. The capacity of a pure capacitor is 1 farad . In dc circuits, its effective resistance will be

- (a) Zero (b) Infinite
 (c) 1 ohm (d) $1/2 \text{ ohm}$

71. In an ac circuit, the current lags behind the voltage by $\pi / 3$. The components in the circuit are

- (a) R and L (b) R and C
 (c) L and C (d) Only R

72. The reactance of a coil when used in the domestic ac power supply (220 volts , $50 \text{ cycles per second}$) is 50 ohms . The inductance of the coil is nearly

- (a) 2.2 henry (b) 0.22 henry
 (c) 1.6 henry (d) 0.16 henry

73. In an ac circuit, the power factor


- (a) Is zero when the circuit contains an ideal resistance only
 (b) Is unity when the circuit contains an ideal resistance only
 (c) Is zero when the circuit contains an ideal inductance only
 (d) Is unity when the circuit contains an ideal inductance only

74. A resistance of 40 ohm and an inductance of 95.5 millihenry are connected in series in a 50 cycles/second ac circuit. The impedance of this combination is very nearly

- (a) 30 ohm (b) 40 ohm
 (c) 50 ohm (d) 60 ohm

75. For high frequency, a capacitor offers
 (a) More reactance (b) Less reactance
 (c) Zero reactance (d) Infinite reactance
76. The coil of choke in a circuit
 (a) Increases the current
 (b) Decreases the current
 (c) Does not change the current
 (d) Has high resistance to dc circuit
77. In a circuit, the current lags behind the voltage by a phase difference of $\pi/2$. The circuit contains which of the following
 (a) Only R (b) Only L
 (c) Only C (d) R and C
78. The inductive reactance of an inductor of $\frac{1}{\pi}$ henry at 50 Hz frequency is
 (a) $\frac{50}{\pi}$ ohm (b) $\frac{\pi}{50}$ ohm
 (c) 100 ohm (d) 50 ohm
79. An oscillator circuit consists of an inductance of 0.5mH and a capacitor of 20 μF . The resonant frequency of the circuit is nearly
 (a) 15.92 Hz (b) 159.2 Hz
 (c) 1592 Hz (d) 15910 Hz
80. Reactance of a capacitor of capacitance $C \mu F$ for ac frequency $\frac{400}{\pi}$ Hz is 25Ω . The value C is
 (a) 50 μF (b) 25 μF
 (c) 100 μF (d) 75 μF
81. The power factor of an ac circuit having resistance (R) and inductance (L) connected in series and an angular velocity ω is
 (a) $R/\omega L$ (b) $R/(R^2 + \omega^2 L^2)^{1/2}$
 (c) $\omega L/R$ (d) $R/(R^2 - \omega^2 L^2)^{1/2}$
82. A circuit has a resistance of 11 Ω , an inductive reactance of 25 Ω and a capacitive resistance of 18 Ω . It is connected to an ac source of 260V and 50Hz. The current through the circuit (in amperes) is
 (a) 11 (b) 15
 (c) 18 (d) 20
83. A 0.7 henry inductor is connected across a 120V – 60 Hz ac source. The current in the inductor will be very nearly
 (a) 4.55 amp (b) 0.355 amp
 (c) 0.455 amp (d) 3.55 amp
84. There is a 5 Ω resistance in an ac, circuit. Inductance of 0.1H is connected with it in series. If equation of ac e.m.f. is $5 \sin 50t$ then the phase difference between current and e.m.f. is
 (a) $\frac{\pi}{2}$ (b) $\frac{\pi}{6}$
 (c) $\frac{\pi}{4}$ (d) 0
85. An inductor of inductance L and resistor of resistance R are joined in series and connected by a source of frequency ω . Power dissipated in the circuit is
 (a) $\frac{(R^2 + \omega^2 L^2)}{V}$ (b) $\frac{V^2 R}{(R^2 + \omega^2 L^2)}$
 (c) $\frac{V}{(R^2 + \omega^2 L^2)}$ (d) $\frac{\sqrt{R^2 + \omega^2 L^2}}{V^2}$
86. In a ac circuit of capacitance the current from potential is
 (a) Forward
 (b) Backward
 (c) Both are in the same phase

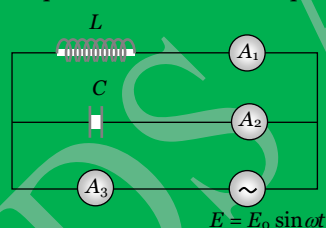
- (d) None of these
87. A coil of 200Ω resistance and 1.0 H inductance is connected to an ac source of frequency $200/2\pi\text{ Hz}$. Phase angle between potential and current will be
 (a) 30° (b) 90°
 (c) 45° (d) 0°
88. In a LCR circuit the pd between the terminals of the inductance is 60 V , between the terminals of the capacitor is 30 V and that between the terminals of resistance is 40 V . the supply voltage will be equal to
 (a) 50 V (b) 70 V
 (c) 130 V (d) 10 V
89. Radio frequency choke uses core of
 (a) Air (b) Iron
 (c) Air and iron (d) None of these
90. In a LCR circuit capacitance is changed from C to $2C$. For the resonant frequency to remain unchanged, the inductance should be change from L to
 (a) $4L$ (b) $2L$
 (c) $L/2$ (d) $L/4$
91. In an LCR series ac circuit, the voltage across each of the components, L , C and R is 50 V . the voltage across the LC combination will be
 (a) 50 V (b) $50\sqrt{2}\text{ V}$
 (c) 100 V (d) 0 V (zero)
92. A coil has $L = 0.04\text{ H}$ and $R = 12\Omega$. When it is connected to 220 V , 50 Hz supply the current flowing through the coil, in amperes is
 (a) 10.7 (b) 11.7
 (c) 14.7 (d) 12.7
93. The current in series LCR circuit will be maximum when ω is
 (a) As large as possible
 (b) Equal o natural frequency of LCR system
 (c) \sqrt{LC}
 (d) $\sqrt{1/LC}$
94. An inductor L and a capacitor C are connected in the circuit as shown in the figure. The frequency of the power supply is equal to the resonant frequency of the circuit. Which ammeter will read zero ampere



- (a) A_1 (b) A_2
 (c) A_3 (d) None of these
95. Which of the following components of a LCR circuit, with ac supply, dissipates energy
 (a) L (b) R
 (c) C (d) All of these
96. In a circuit L , C and R are connected in series with an alternating voltage source of frequency f . The current leads the voltage by 45° . The value of C is
 (a) $\frac{1}{2\pi f(2\pi fL + R)}$
 (b) $\frac{1}{\pi f(2\pi fL + R)}$
 (c) $\frac{1}{2\pi f(2\pi fL - R)}$

(d) $\frac{1}{\pi f(2\pi fL - R)}$

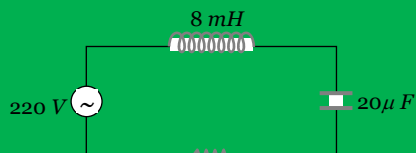97. In an A.C. circuit the current
 (a) Always leads the voltage
 (b) Always lags behind the voltage
 (c) Is always in phase with the voltage
 (d) May lead or lag behind or be in phase with the voltage
98. For the series LCR circuit shown in the figure, what is the resonance frequency and the amplitude of the current at the resonating frequency




- (a) $2500 \text{ rad} - s^{-1}$ and $5\sqrt{2} \text{ A}$
 (b) $2500 \text{ rad} - s^{-1}$ and 5 A
 (c) $2500 \text{ rad} - s^{-1}$ and $\frac{5}{\sqrt{2}} \text{ A}$
 (d) $25 \text{ rad} - s^{-1}$ and $5\sqrt{2} \text{ A}$

EXERCISE 3


1. When 100 volts dc is supplied across a solenoid, a current of 1.0 amperes flows in it. When 100 volts ac is applied across the same coil, the current drops to 0.5 ampere. If the frequency of ac source is 50 Hz, then the impedance and inductance of the solenoid are
 (a) 200Ω and 0.55 henry (b) 100Ω and 0.86 henry
 (c) 200Ω and 1.0 henry (d) 100Ω and 0.93 henry
2. In an LR-circuit, the inductive reactance is equal to the resistance R of the circuit. An e.m.f. $E = E_0 \cos(\omega t)$ applied to the circuit. The power consumed in the circuit is

- (a) $\frac{E_0^2}{R}$ (b) $\frac{E_0^2}{2R}$
 (c) $\frac{E_0^2}{4R}$ (d) $\frac{E_0^2}{8R}$

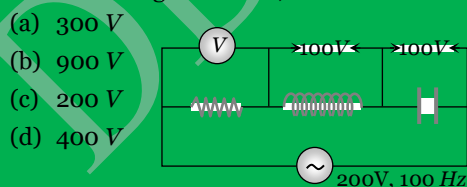3. One 10 V, 60 W bulb is to be connected to 100 V line. The required induction coil has self inductance of value ($f = 50 \text{ Hz}$)
 (a) 0.052 H (b) 2.42 H
 (c) 16.2 mH (d) 1.62 mH
4. In the circuit given below, what will be the reading of the voltmeter




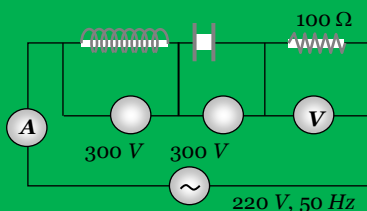5. In the circuit shown below, what will be the readings of the voltmeter and ammeter




- (a) 800 V, 2A (b) 300 V, 2A

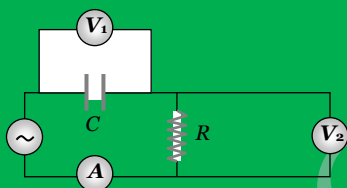- (c) 220 V, 2.2 A (d) 100 V, 2 A
6. A bulb and a capacitor are connected in series to a source of alternating current. If its frequency is increased, while keeping the voltage of the source constant, then
- (a) Bulb will give more intense light
 (b) Bulb will give less intense light
 (c) Bulb will give light of same intensity as before
 (d) Bulb will stop radiating light
7. An alternating e.m.f. of angular frequency ω is applied across an inductance. The instantaneous power developed in the circuit has an angular frequency
- (a) $\frac{\omega}{4}$ (b) $\frac{\omega}{2}$
 (c) ω (d) 2ω
8. The voltage of an ac source varies with time according to the equation $V = 100 \sin 100\pi \cos 100\pi$ where t is in seconds and V is in volts. Then
- (a) The peak voltage of the source is 100 volts
 (b) The peak voltage of the source is 50 volts
 (c) The peak voltage of the source is $100 / \sqrt{2}$ volts
 (d) The frequency of the source is 50 Hz
9. The diagram shows a capacitor C and a resistor R connected in series to an ac source. V_1 and V_2 are voltmeters and A is an ammeter




Consider now the following statements

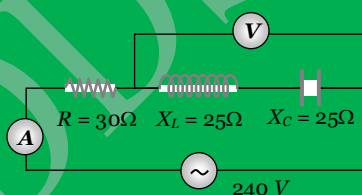- I. Readings in A and V_2 are always in phase
 II. Reading in V_1 is ahead in phase with reading in V_2
 III. Readings in A and V_1 are always in phase which of these statements are/is correct
- (a) I only (b) II only
 (c) I and II only (d) II and III only
10. In the circuit shown in figure neglecting source resistance the voltmeter and ammeter reading will respectively, will be



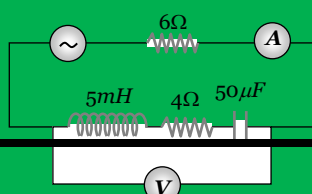- (a) 0V, 3A (b) 150V, 3A
 (c) 150V, 6A (d) 0V, 8A
11. The voltage of an ac supply varies with time (t) as $V = 120 \sin 100 \pi t \cos 100 \pi t$. The maximum voltage and frequency respectively are
- (a) 120 volts, 100 Hz (b) $\frac{120}{\sqrt{2}}$ volts, 100 Hz
 (c) 60 volts, 200 Hz (d) 60 volts, 100 Hz
12. In the circuit shown in the figure, the ac source gives a voltage $V = 20 \cos(2000 t)$. Neglecting source resistance, the voltmeter and ammeter reading will be



- (a) $0V, 0.47A$ (b) $1.68V, 0.47A$
 (c) $0V, 1.4A$ (d) $5.6V, 1.4A$

13. A telephone wire of length 200 km has a capacitance of $0.014\text{ }\mu\text{F}$ per km . If it carries an ac of frequency 5 kHz , what should be the value of an inductor required to be connected in series so that the impedance of the circuit is minimum
 (a) 0.35 mH (b) 35 mH
 (c) 3.5 mH (d) Zero


14. In a certain circuit current changes with time according to $i = 2\sqrt{t}$. *r.m.s.* value of current between $t = 2$ to $t = 4\text{ s}$ will be
 (a) $3A$ (b) $3\sqrt{3}A$
 (c) $2\sqrt{3}A$ (d) $(2 - \sqrt{2})A$

15. Match the following

Currents	<i>r.m.s.</i> values
(1) $x_0 \sin \omega t$	(i) x_0
(2) $x_0 \sin \omega t \cos \omega t$	(ii) $\frac{x_0}{\sqrt{2}}$
(3) $x_0 \sin \omega t + x_0 \cos \omega t$	(iii) $\frac{x_0}{(2\sqrt{2})}$
(a) 1. (i), 2. (ii), 3. (iii)	(b) 1. (ii), 2. (iii), 3. (i)
(c) 1. (i), 2. (iii), 3. (ii)	(d) None of these

16. The reading of ammeter in the circuit shown will be

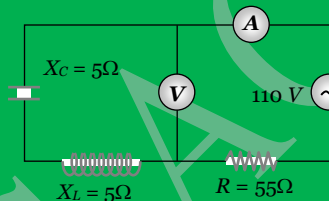- (a) $2A$
 (b) $2.4A$
 (c) Zero
 (d) $1.7A$



17. An ac source of angular frequency ω is fed across a resistor r and a capacitor C in series. The current registered is I . If now the frequency of source is changed to $\omega/3$ (but maintaining the same voltage), the current in then circuit is found to be halved. Calculate the ratio of reactance to resistance at the original frequency ω

- (a) $\sqrt{\frac{3}{5}}$ (b) $\sqrt{\frac{2}{5}}$
 (c) $\sqrt{\frac{1}{5}}$ (d) $\sqrt{\frac{4}{5}}$

18. An *LCR* series circuit with a resistance of 100 ohm is connected to an ac source of 200 V (*r.m.s.*) and angular frequency 300 rad/s . When only the capacitor is removed, the current lags behind the voltage by 60° . When only the inductor is removed the current leads the voltage by 60° . The average power dissipated is

- (a) 50 W (b) 100 W
 (c) 200 W (d) 400 W

19. A virtual current of $4A$ and 50 Hz flows in an ac circuit containing a coil. The power consumed in the coil is 240 W . If the virtual voltage across the coil is 100 V its inductance will be


- (a) $\frac{1}{3\pi}\text{ H}$ (b) $\frac{1}{5\pi}\text{ H}$
 (c) $\frac{1}{7\pi}\text{ H}$ (d) $\frac{1}{9\pi}\text{ H}$

20. For a series *RLC* circuit $R = X_L = 2X_C$. The impedance of the circuit and phase difference (between) V and i will be

- (a) $\frac{\sqrt{5}R}{2}, \tan^{-1}(2)$ (b) $\frac{\sqrt{5}R}{2}, \tan^{-1}\left(\frac{1}{2}\right)$
 (c) $\sqrt{5}X_C, \tan^{-1}(2)$ (d) $\sqrt{5}R, \tan^{-1}\left(\frac{1}{2}\right)$


21. In the adjoining ac circuit the voltmeter whose reading will be zero at resonance is

- (a) V_1
 (b) V_2
 (c) V_3
 (d) V_4

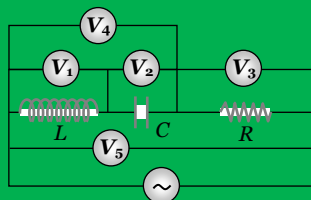

22. In the adjoining figure the impedance of the circuit will be

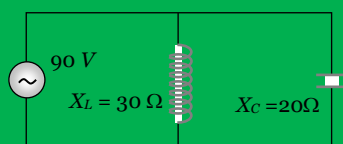- (a) 120 ohm
 (b) 50 ohm
 (c) 60 ohm
 (d) 90 ohm




23. If $i = t^2$ $0 < t < T$ then r.m.s. value of current is

- (a) $\frac{T^2}{\sqrt{2}}$ (b) $\frac{T^2}{2}$
 (c) $\frac{T^2}{\sqrt{5}}$ (d) None of these

24. Is it possible

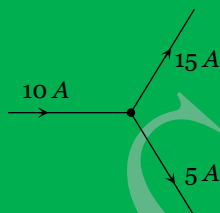- (a) Yes
 (b) No
 (c) Cannot be predicted
 (d) Insufficient data to reply



25. In a series circuit $C = 2\mu F$, $L = 1mH$ and $R = 10\Omega$, when the current in the circuit is maximum, at that time the ratio of the energies stored in the capacitor and the inductor will be

- (a) 1 : 1 (b) 1 : 2
 (c) 2 : 1 (d) 1 : 5

ANSWER KEY

EXERCISE 1

1	b	2	a	3	c	4	b	5	b
6	b	7	c	8	d	9	c	10	c
11	d	12	c	13	b	14	c	15	b
16	d	17	c	18	b	19	d	20	c
21	c	22	a	23	c	24	d	25	c
26	c	27	d	28	b	29	c	30	d
31	d	32	d	33	b	34	b	35	d
36	c	37	a	38	b	39	a	40	c
41	a	42	d	43	b	44	b	45	c
46	c								

EXERCISE 2

1	b	2	a	3	a	4	b	5	a
6	a	7	b	8	c	9	d	10	b
11	c	12	b	13	b	14	b	15	d

16	b	17	a	18	b	19	a	20	a
21	b	22	d	23	b	24	b	25	a
26	d	27	c	28	b	29	c	30	c
31	c	32	b	33	d	34	a	35	c
36	c	37	c	38	b	39	c	40	d
41	b	42	b	43	a	44	a	45	d
46	c	47	a	48	a	49	c	50	b
51	b	52	c	53	b	54	c	55	c
56	a	57	a	58	b	59	b	60	d
61	a	62	c	63	a	64	bd	65	a
66	a	67	a	68	a	69	a	70	b
71	a	72	d	73	bc	74	c	75	b
76	b	77	b	78	c	79	c	80	a
81	b	82	d	83	c	84	c	85	b
86	a	87	c	88	a	89	a	90	c
91	d	92	d	93	d	94	c	95	b
96	a	97	d	98	b				

EXERCISE 3

1	a	2	c	3	a	4	c	5	c
6	a	7	d	8	b	9	b	10	d
11	d	12	d	13	a	14	c	15	b
16	c	17	a	18	d	19	b	20	b
21	d	22	c	23	c	24	a	25	d